

NCTU-EE IC LAB – Spring 2018

Lab01 Exercise

Design: Booth Multiplier

Data Preparation

1. Extract test data from TA's directory:
`% tar xvf ~iclabta01/Lab01.tar`
2. The extracted LAB directory contains:
 - a. Practice/ : example code
 - b. Exercise/ : your design

Design Description and Examples

Booth algorithm is a multiplication operation that multiplies two numbers in two's complement notation. The detail algorithm is described as below:

1. Find the second and the third biggest of the five inputs and execute with Booth algorithm.
2. Assume that the multiplicand m is x -bit and multiplier r is y -bit. Initialize a register P for the final result, and the length is $x+y+1$ bits. The initial value of P is $0(x \text{ bits})_r(y \text{ bits})_0(1 \text{ bit})$.
3. The rightmost 2 bits used for the selection of different executions.

| LSB | Execution |
|-----|--|
| 00 | No execution |
| 01 | Add m to the left part of P |
| 10 | Subtract m from the left part of P |
| 11 | No execution |

4. **Arithmetically shift** 1 bit on P
5. Repeat the step (3) and (4) for y times.
6. The final answer is obtained by dropping the LSB from P .

The summary of the description and specifications are as followings:

| Input Signal | Bit Width | Description |
|--------------|-----------|--------------|
| in_1 | 6 | signed input |
| in_2 | 6 | signed input |
| in_3 | 6 | signed input |

| | | |
|----------------------|------------------|--------------------|
| in_4 | 6 | signed input |
| in_5 | 6 | signed input |
| Output Signal | Bit Width | Description |
| out | 12 | Product |

Examples:

Assume in_1 = 0000 , in_2 = 0010 , in_3 = 0111 , in_4 = 0110 , in_5 =0001

The third biggest input is 0010,and the second biggest input is 0110

0010*0110

| Iteration | Multiplicand | Execution | P |
|-----------|--------------|---|--------------------|
| 0 | 0010 | initial | 0000_0110_0 |
| 1 | 0010 | LSB:00 no execution | 0000_01100 |
| | 0010 | Arithmetically shift 1 bit on P | 0000_00110 |
| 2 | 0010 | LSB:10 Subtract m from the left part of P. | 1110_00110 |
| | 0010 | Arithmetically shift 1 bit on P | 1111_00011 |
| 3 | 0010 | LSB:11 no execution | 1111_00011 |
| | 0010 | Arithmetically shift 1 bit on P | 1111_10001 |
| 4 | 0010 | LSB:01 Add m to the left part of P. | 0001_10001 |
| | 0010 | Arithmetically shift 1 bit on P | 0000_11000 |

Out = 0000_1100

Inputs

1. The signal in_1, in_2, in_3, in_4,in_5 are signed 6-bit inputs.

Outputs

The signal **out** is signed 12-bit. This represents the product of two input.

Specifications


1. You can **ONLY** use Booth algorithm to complete the multiplication .
2. Top module name : Booth (File name: Booth.v)
3. Input pins : in_1[5:0], in_2[5:0], in_3[5:0], in_4[5:0], in_5[5:0],
4. Output pins : out[11:0]
5. The maximal delay is **15ns**. You can choose the delay you want, but it must be less than 15ns. The delay of your design will influence your grade.

Note: Change the parameter **Max_Delay** in 02_SYN/syn.tcl if you want to compress your cycle time.

```
#-----  
# Global Parameters  
#-----  
set DESIGN "Booth"  
set MAX_Delay 10
```

6. After synthesis, check the “Booth.area” and “Booth.timing” in the folder “Report”. The area report is valid only when the slack in the end of “Booth.timing” is non-negative.
7. The synthesis result **cannot** contain any **latch**.
Note: You can check if there is a latch by searching the keyword “**Latch**” in 02_SYN/syn.log

Block Diagram

 

Grading Policy

The performance is determined by the area and delay of your design. The less cost your design has, the higher grade you get.

Function Validity: 70%

Performance: 30% (Total simulation time: 15%, area: 15%)

Note

1. Please upload the following file on e3 platform before **12:00 at noon on Sep. 25**:
Booth_iclab??v and **latency_iclab??txt** (latency is the smallest latency you use)

in synthesis, ?? is your account no.)

Ex: Booth_iclab99.v, 5.5_iclab99.txt

2. Template folders and reference commands:

In RTL simulation, the name of template folder and reference commands is:

01_RTL:

“./01_run”

02_SYN/ (Synthesis):

./01_run_dc

(Check **latch** by searching the keyword “**Latch**” in 02_SYN/syn.log)

(Check the design’s timing in /Report/Booth.timing)

03_GATE_SIM/ (GL simulation):

./01_run

You can key in **./09_clean_up** to clear all log files and dump files in each folder

Example Waveform

Input and output signal:

